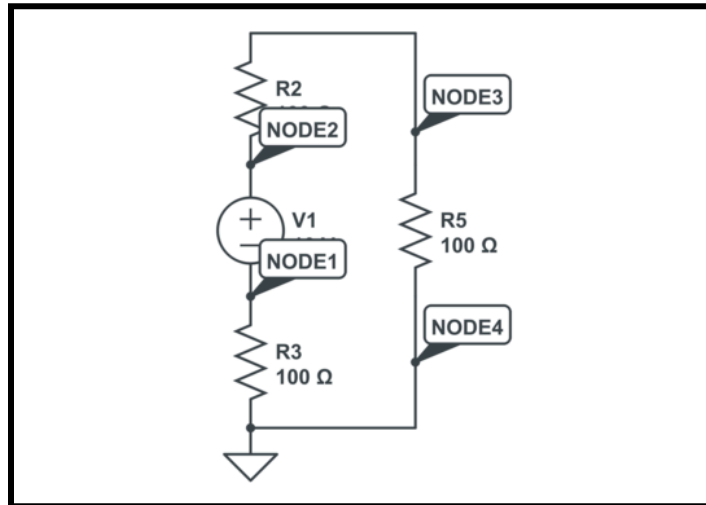


1. Resistors in Series

c. Node 1 -5V, Node 2 5V, Node 3 0V, Current 50 mA


d. Node 1 -3.33V, Node 2 6.67V, Node 3, 3.33V, Node 4 0V, Current 33.33 mA



2. Resistors in Parallel


c. Node 1: 10V and 200mA, Node 2: 0V and 200mA, Node 3: 10V and 100 mA, Node: 4 0V and 100mA, Node 5: 10V and 100mA, Node 6: 0V and 100mA.

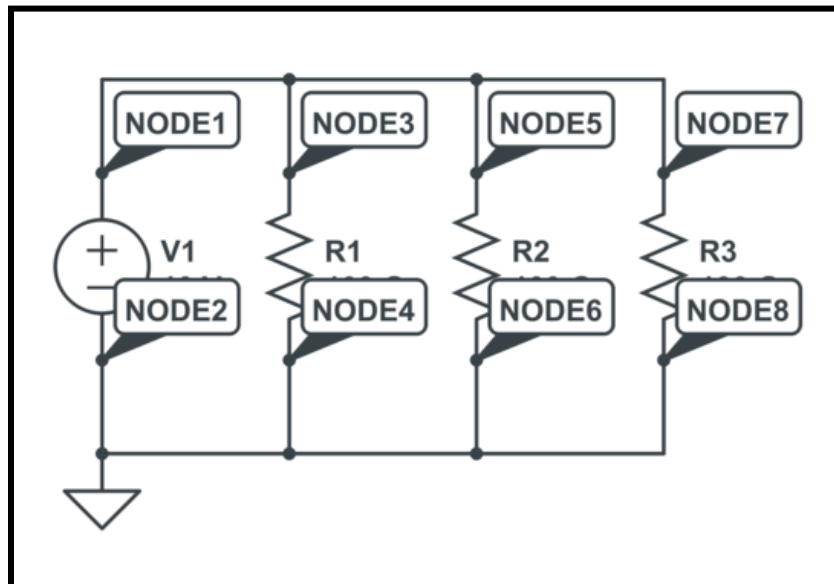d. Node 1: 10V and 300mA, Node2: 0V and 200mA, Node3: 10V and 100mA, Node4: 0V and 100mA, Node 5: 10V and 100mA, Node 6: 0V and 100mA, Node 7: 10V and 100mA, Node 8: 0V and 100mA




3. Resistors in Series and Parallel


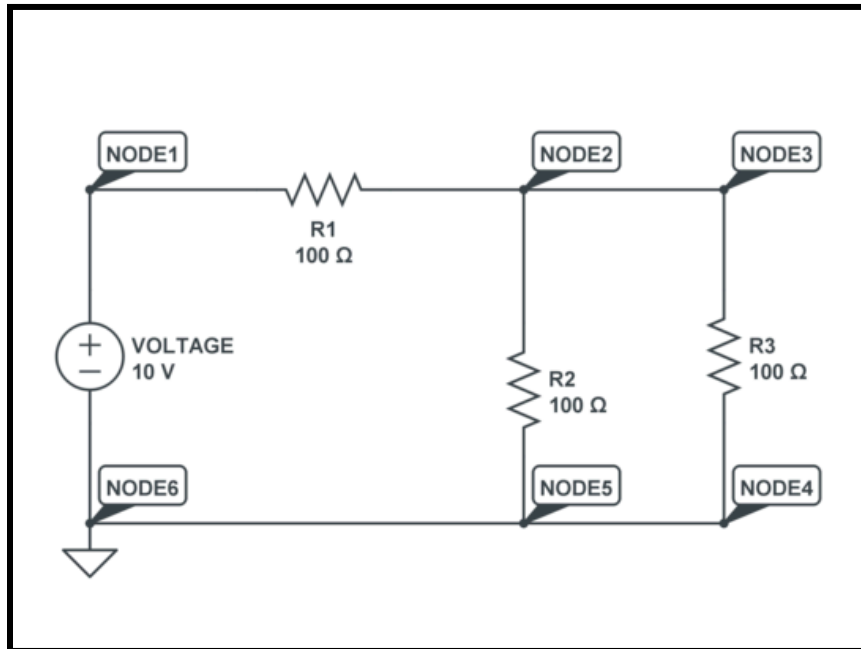
c. Node 1: 10V and 66.6 mA, Node 2: 3.33V and 66.6 mA, Node 3: 3.33V and 33.3 mA,
Node 4: 0V and 33.3 mA, Node 5: 0V and 33.3 mA, Node 6: 0V and 66.6 mA.



4. Powering Light Bulbs


a. 1.0 W

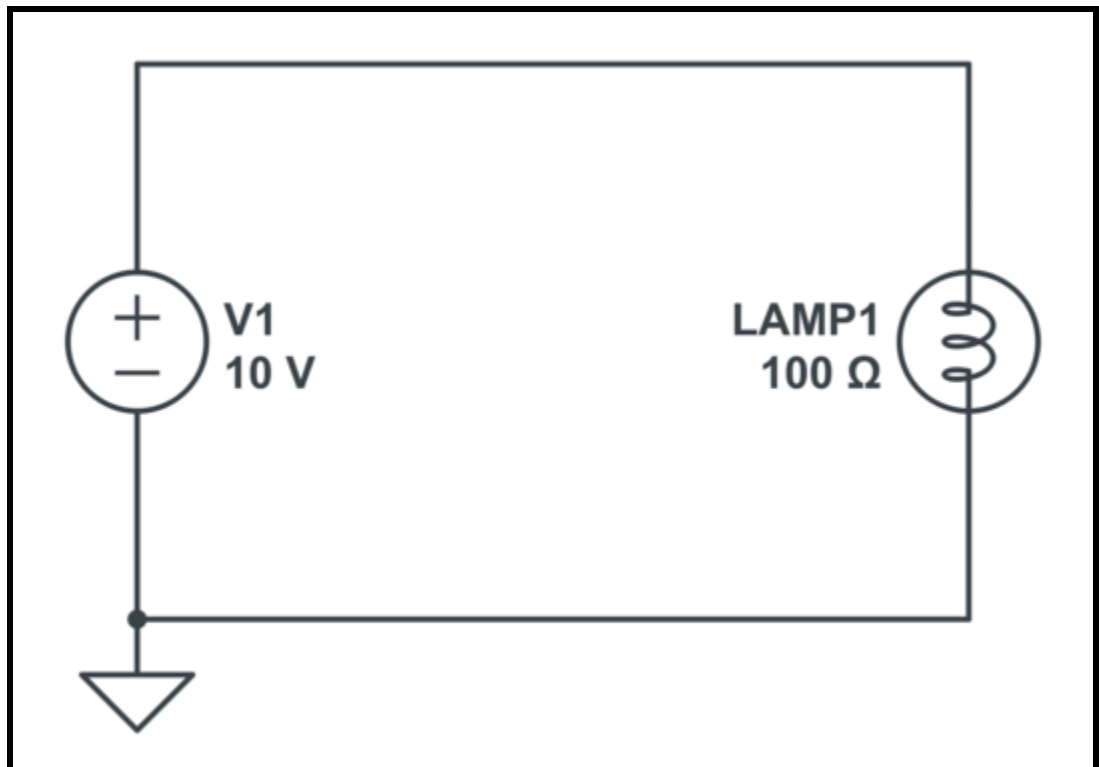

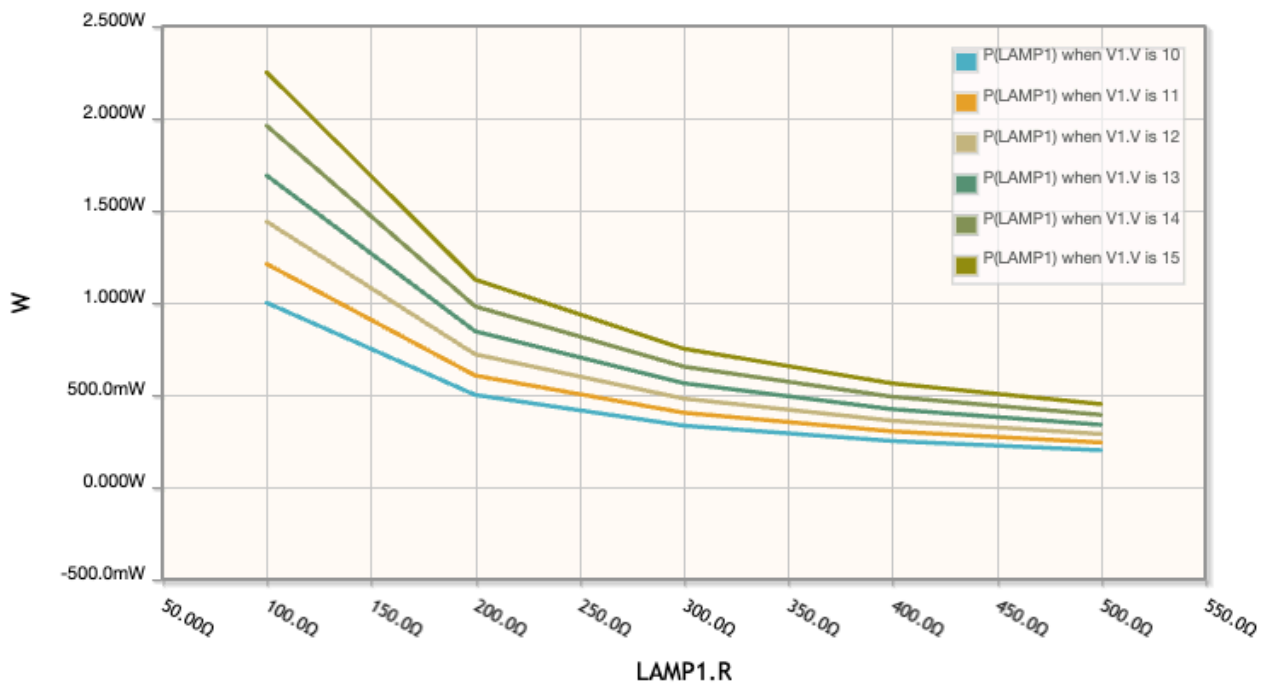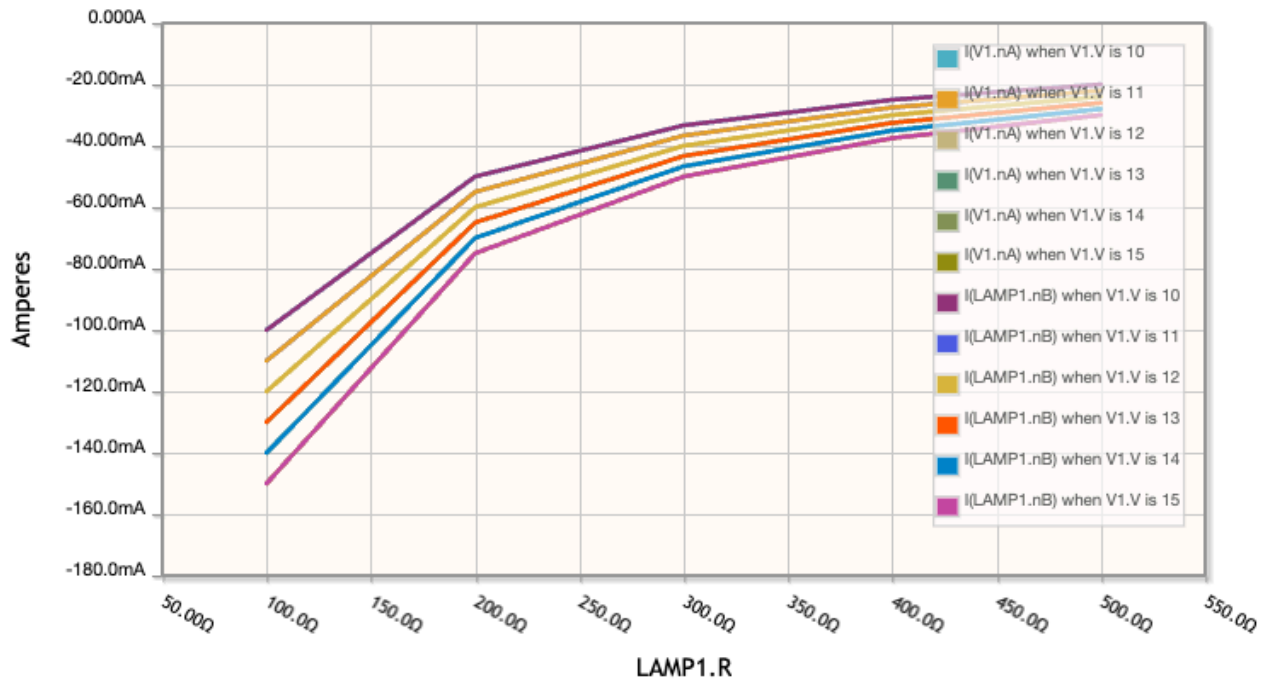


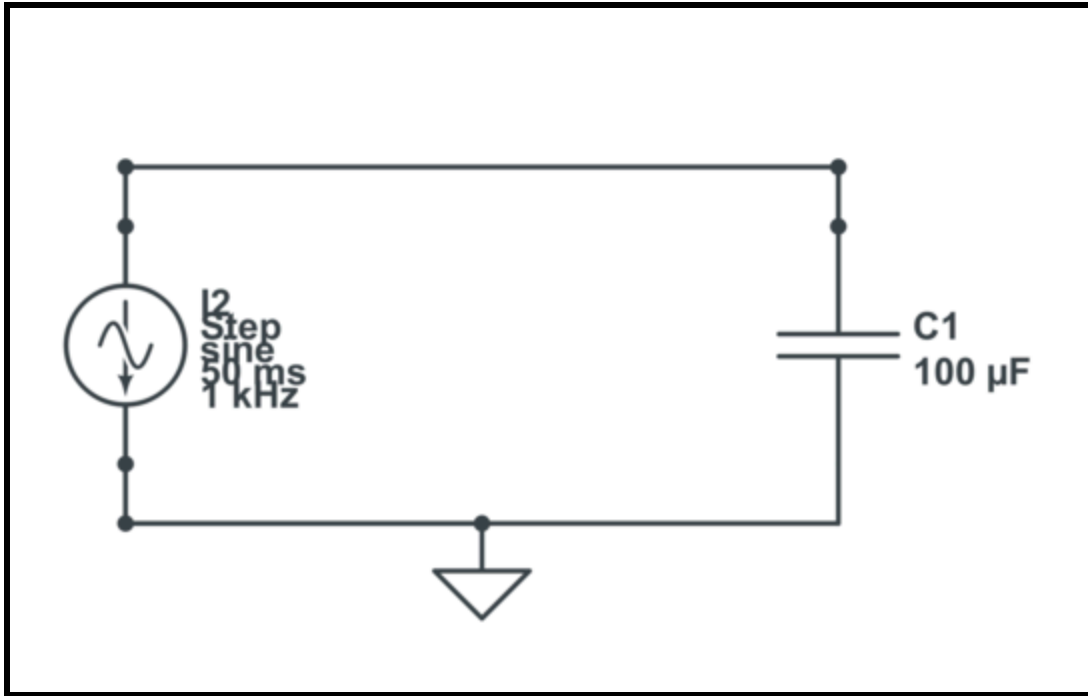
5. Capacitor Circuit

Tried with several different values for the capacitor as well, saw similar trends different amounts, etc.





a.


For Sine:

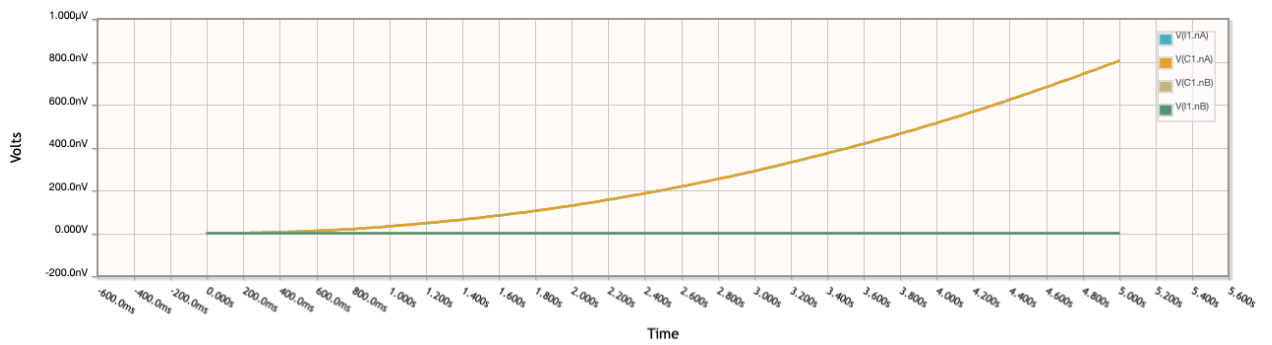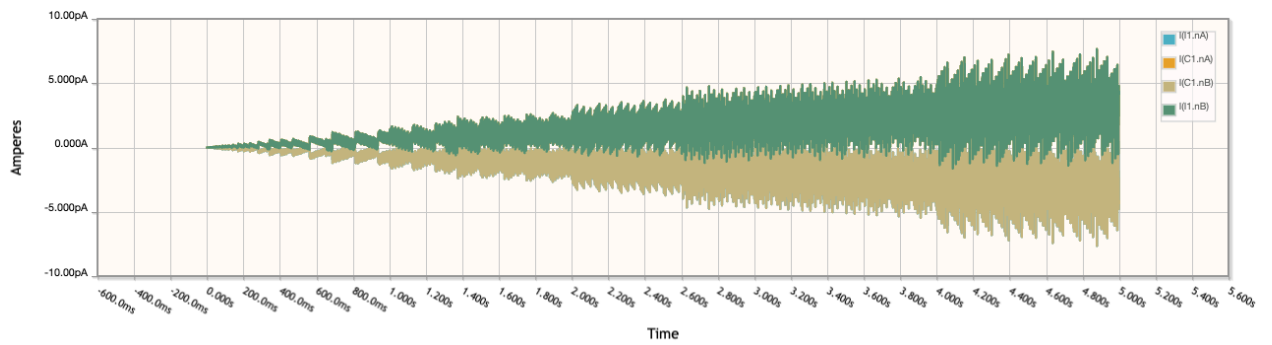


For Step:

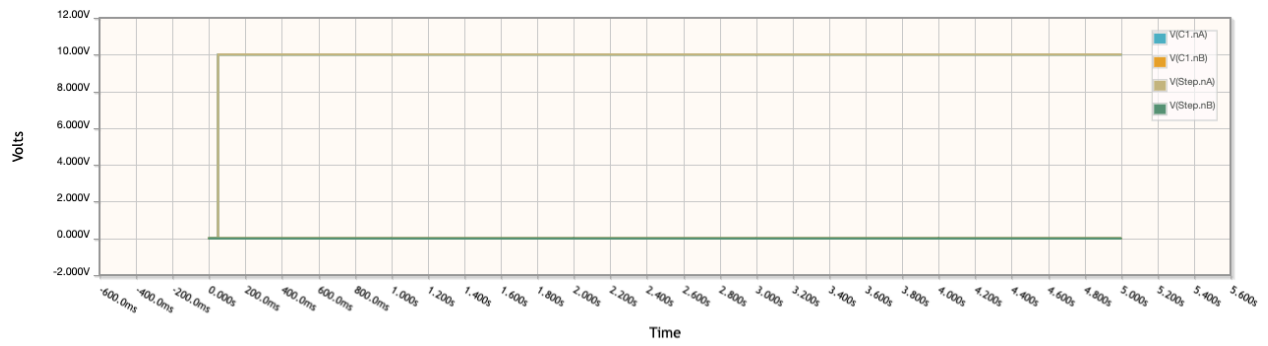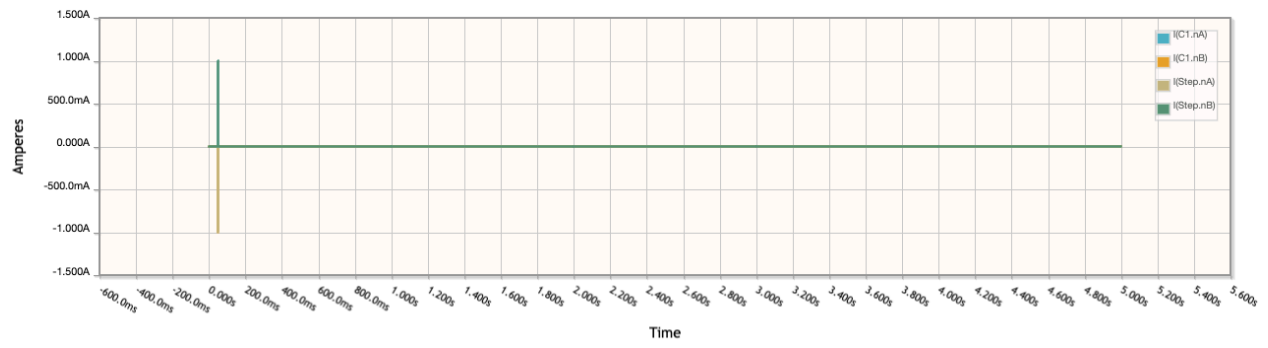


6. RC Circuit

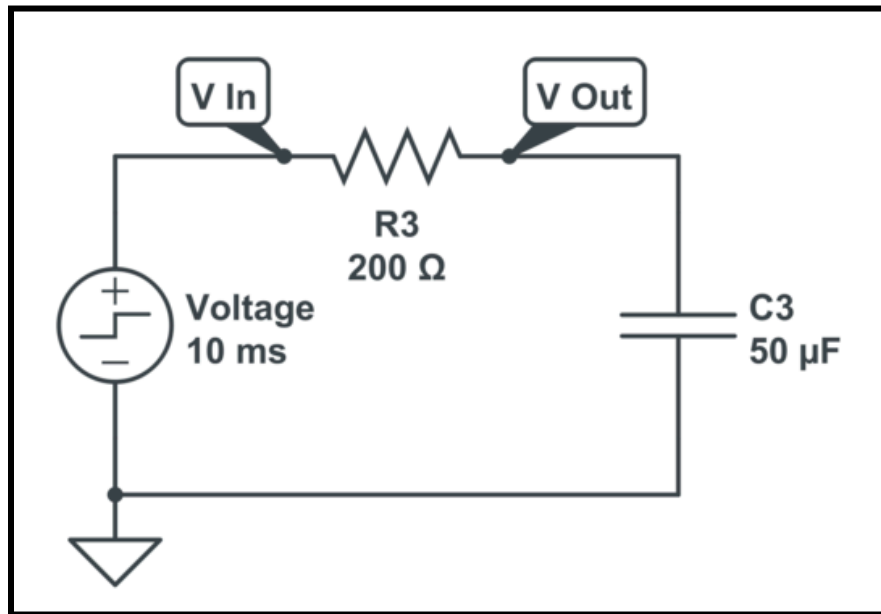

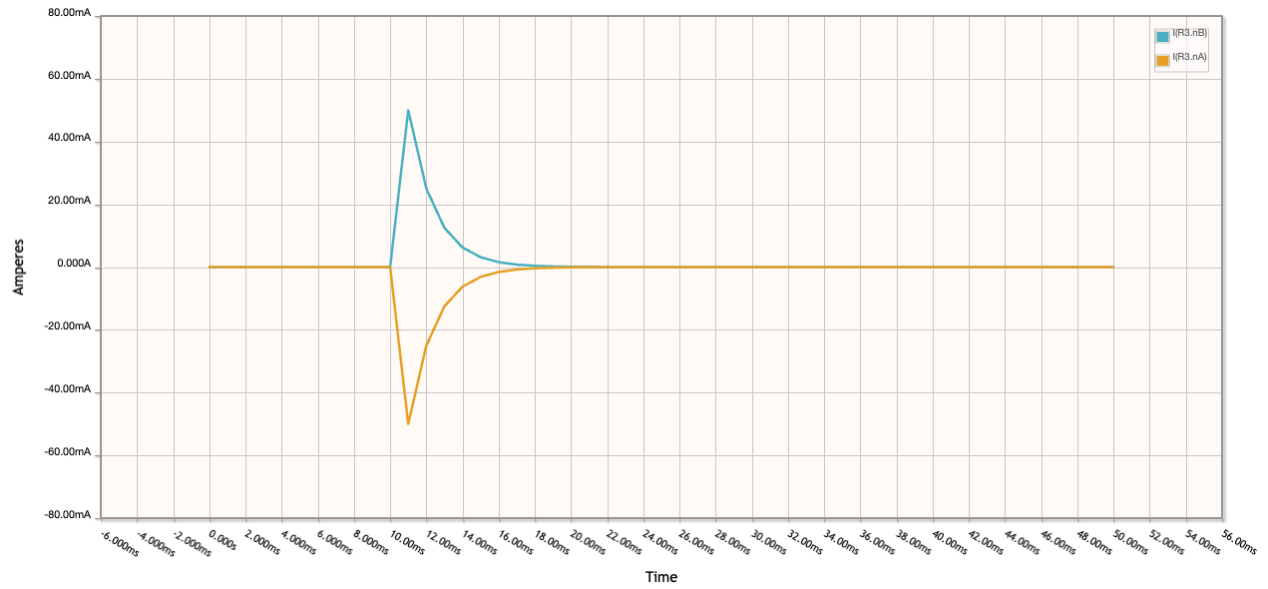

100Ω Resistor and 10μF Capacitor

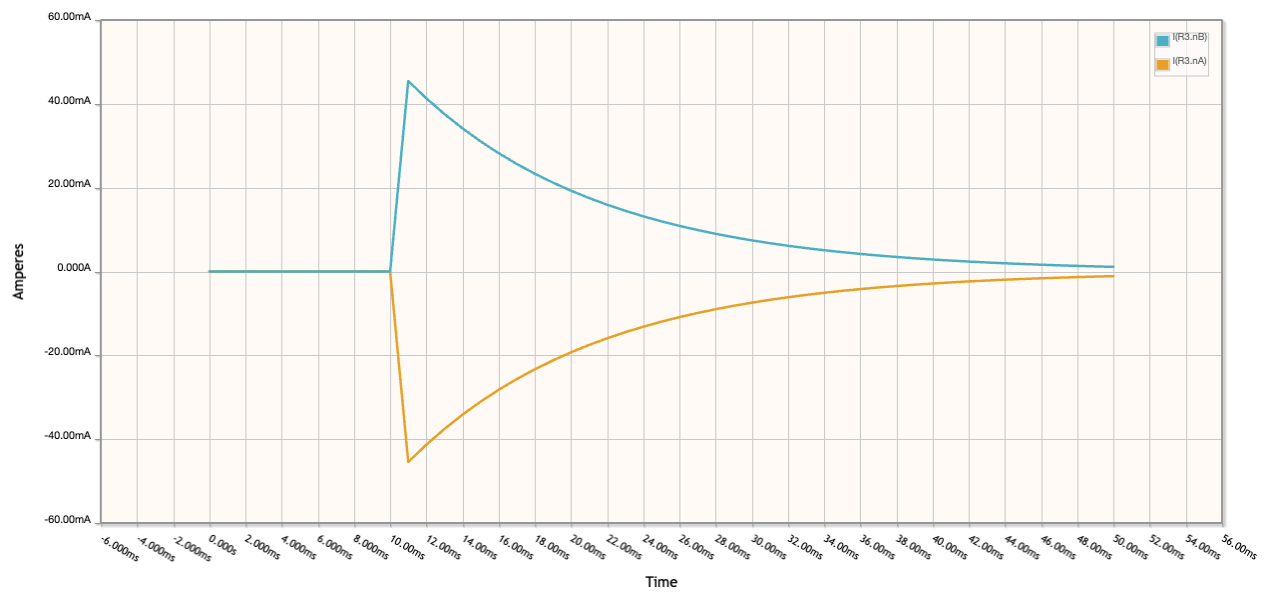

200Ω Resistor and 50μF Capacitor

7. RC Filter

a. Input voltage is 0V, output voltage is 0V.

